
7447
Here we are usind 7474 ic to increment the number

pin diagrame of 7474 ic:

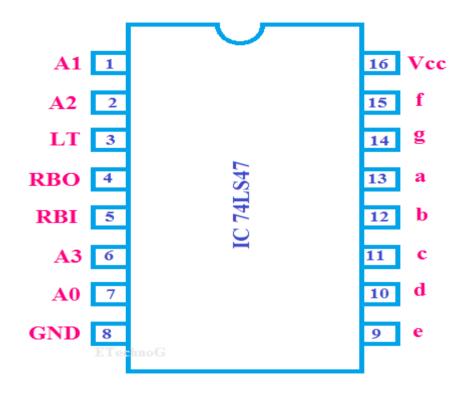

Connections:

7447	a	b	С	d	e	f	g
sevenseg	a	b	С	d	e	f	g

7447	A0	A1	A2	A3	GND	Vcc
Arduino	2	3	4	5	GND	5v

Code:

```
int Z=0,Y=0,X=1,W=1;
int D,C,B,A;


//Code released under GNU GPL. Free to use for anything.
void disp_7447(int D, int C, int B, int A)
{
    digitalWrite(2, A); //LSB
```

```
digitalWrite(3, B);
digitalWrite(4, C);
digitalWrite(5, D); //MSB
// the setup function runs once when you press reset or power the board
void setup() {
 pinMode(2, OUTPUT);
 pinMode(3, OUTPUT);
 pinMode(4, OUTPUT);
 pinMode(5, OUTPUT);
// the loop function runs over and over again forever
void loop() {
Z) ||(!W\&\&!X\&\&!Y\&\&Z);
Z);
C = (W \& X \& \& ! Y \& \& ! Z) || (!W \& \& ! X \& \& Y \& \& ! Z) || (W \& \& X \& \& Y \& \& ! Z) || (!W \& X \& \& X \& \& Y \& \& ! Z);
D = (W\&\&X\&\&Y\&\&!Z)||(!W\&\&!X\&\&!Y\&\&Z);
disp_{7447}(D,C,B,A);
```

Truth Table:

Z	Y	X	W	D	С	В	A
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1

Output:

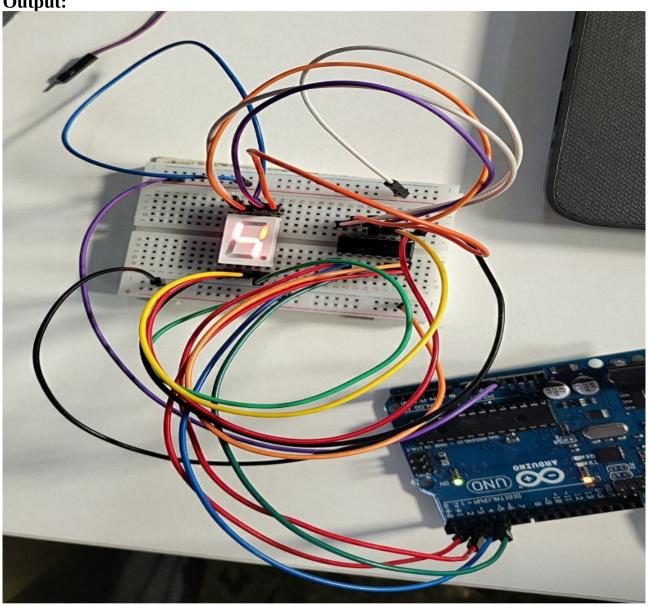

- Q.Now write a program where
- (a) the binary inputs are given by connecting to 0 and 1 on the breadboard
- (b) incremented by 1 using Table and
- (c) the incremented value is displayed on the seven segment display.

Code:

//Declaring all variables as integers int *Z*,*Y*,*X*,*W*; int *D*,*C*,*B*,*A*;

//Code released under GNU GPL. Free to use for anything. void disp_7447(int D, int C, int B, int A)

```
digitalWrite(2, A); //LSB
    digitalWrite(3, B);
    digitalWrite(4, C);
    digitalWrite(5, D); //MSB
// the setup function runs once when you press reset or power the board
void setup() {
         pinMode(2, OUTPUT);
         pinMode(3, OUTPUT);
         pinMode(4, OUTPUT);
         pinMode(5, OUTPUT);
         pinMode(6, INPUT);
         pinMode(7, INPUT);
         pinMode(8, INPUT);
         pinMode(9, INPUT);
// the loop function runs over and over again forever
void loop() {
     W = digitalRead(6);
    X = digitalRead(7);
     Y = digitalRead(8);
    Z = digitalRead(9);
    Z) ||(!W\&\&!X\&\&!Y\&\&Z);
    B = (W \& \& ! X \& \& ! Y \& \& ! Z) || (! W \& \& X \& \& \& ! Y \& \& ! Z) || (W \& \& X \& \& Y \& \& \& X \&
Z);
    C = (W \& X \& \& ! Y \& \& ! Z) || (!W \& \& ! X \& \& Y \& \& ! Z) || (W \& \& X \& \& Y \& \& ! Z) || (!W \& X \& \& X \& \& Y \& \& ! Z);
    D = (W \& X \& Y \& \& Y \& \& ! Z) | | (!W \& \& !X \& \& !Y \& \& Z);
disp_7447(D,C,B,A);
```

note: Here inputs are changing manually